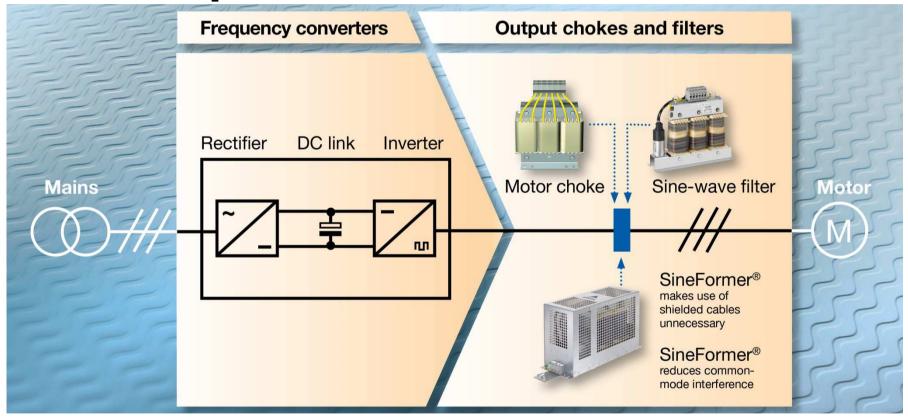




EMC Output Filter Solutions



EPCOS AG


A TDK Group Company Magnetics Business Group • Power EMC Filters Munich, Germany April 2016

Output filter concepts


dv/dt chokes

B86301U*R000/S000



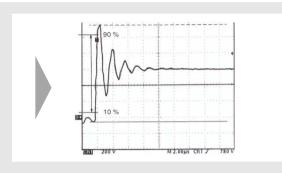


Strong reduction of dv/dt

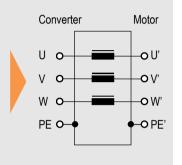


Sine-wave filters

B84143V*R227/R229/R230

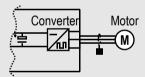

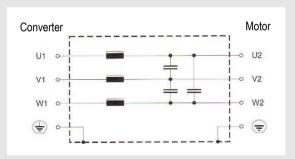
Shielded motor line necessary for dv/dt and sine-wave filters



Forms sine wave between the phases

BUT

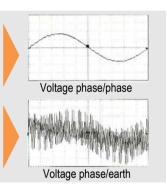
Common-mode Interference is still present



Sine-wave EMC filters


B84143V*R127

SineFormer®

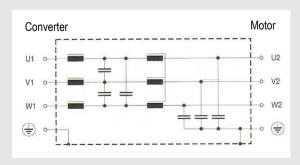

Forms sine wave between the phases

Reduces commonmode interference

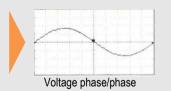

Eliminates need for shielded motor cables and reduces motor bearing currents!

Output filter concepts: Advantages & disadvantages

| | toi / taraintagoo a aloaaraintagoo |
|-----------------------|--|
| | Reduce dv/dt peaks significantly |
| | Low-cost solution |
| dv/dt chokes | Motor line is limited to approx. 100 m |
| | No reduction of acoustic noise |
| | Shielded motor cables necessary |
| | Reduce dv/dt peaks significantly |
| | Forms sine wave between the phases |
| Sine-wave filters | Reduction of acoustic motor noise created by clock frequency |
| | Reduction of eddy current losses |
| | Shielded motor cables necessary |
| | Reduce dv/dt peaks significantly |
| | Forms sine wave between the phases |
| SineFormer® | Reduction of acoustic motor noise created by clock frequency |
| Sine-wave EMC filters | Reduction of eddy current losses |
| | Shielded motor cables not necessary |
| | Minimization of motor bearing currents |


3-phase motor chokes for drives B86301U*R000/S000

Motor chokes reduce the voltage stress at the motor and the dv/dt increase at the frequency converter output

Features

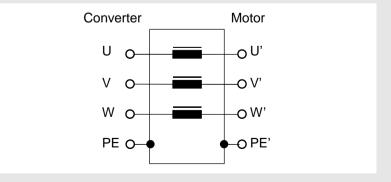- 4 to 1500 A/ 520 V
- 1% impedance reactor
- Easy to install
- Low weight
- Compact design
- Design complies to IEC 60076-6
- UL approved isolation system class F (155 °C)
- IP protection degree IP20 ≤20 A, 24 A ≤IP 10
 ≤112 A, IP 00 >112 A
- Optimized for motor cable lengths up to 100 m
- From stock delivery up to 950 A








Sine-wave output filter series B84143V*R227/ R229/R230

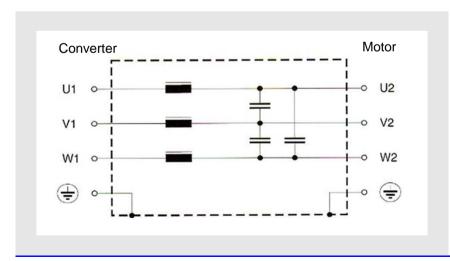- Complete design from 4 A up to 720 A/ 520 V (R227/R230)
- 690 V version: R230 up to 204 A
- Designed for motor cables up to 1000 m
- Slim design unique in the market
- UL approved isolation system
- From stock delivery up to 250 A
- >720 A in development





SineFormer®: Best output filter solution

Commercial advantages

System-cost savings due to the use of unshielded cables

→ Automatic cost savings from a motor-cable length of approx. 100 m

Technical benefits

Longer life cycle of the motor, motor noise reduction, substantial compensation of bearing currents and eddy current losses, no forced ventilation necessary

- → Maintenance-free (fan would have a life cycle of 2 to 4 years only), no feedback to the DC link needed
- → Reduction of all kinds of radiation sources by easy installation

Installation advantage

Unshielded cables are lighter and more flexible

→ Cost savings during installation

Logistics advantage

Shielded cables are used in small volumes which is cost intensive → Unshielded cables are standard products



Compact concept!

Unique on the market!

SineFormer®: Data sheet



- Functional tests up to 1000 m unshielded cable passed
- EMC tests with 300 m unshielded cable passed (radiated emissions)

Ordering code B84143V****R127

Rated voltage 520 VAC (600 V)

Rated current (40 °C) 6 to 180 A (320 A)

Motor frequency 0 to 100 Hz

Clock frequency 4 to 8 kHz

(2.5 kHz/ 320 A)

Protection degree IP20

Approval UL/CSA

(up to 180 Amps, except 6 A and 45 A version)

SineFormer® B84143V*R127: Technical data

Characteristics and ordering codes

| I _R * | Terminal cross section | ΔV | P _L | R _{typ} | Approx. weight | Ordering code | Approval | |
|------------------|-------------------------------|----|----------------|------------------|----------------|-----------------|------------|-------------|
| Α | mm² | % | W | mΩ | kg | | <i>9</i> 1 | c F\ |
| $V_R = 5$ | 20 V AC | | | | | | | |
| 6 | 4 | 7 | 45 | 290 | 9 | B84143V0006R127 | _ | _ |
| 11 | 4 | 5 | 26 | 46 | 9 | B84143V0011R127 | × | × |
| 16 | 6 | 7 | 38 | 32 | 11 | B84143V0016R127 | × | × |
| 33 | 10 | 8 | 92 | 20 | 24 | B84143V0033R127 | × | × |
| 45 | 10 | 8 | 82 | 17 | 28 | B84143V0045R127 | _ | - |
| 66 | 25 | 8 | 160 | 15 | 47 | B84143V0066R127 | × | × |
| 95 | 50 | 10 | 210 | 8 | 99 | B84143V0095R127 | × | × |
| 180 | 150 | 10 | 450 | 6 | 125 | B84143V0180R127 | × | × |
| $V_R = 6$ | 00 V AC | | | | | | | |
| 320 | see dimensional drawing | 10 | 475 | 4 | 195 | B84143V0320R127 | | _ |




SineFormer®: Circuit diagram

- dv/dt reduction
- Sine-wave signal phase to phase
- Current peak reduction


SineFormer® features

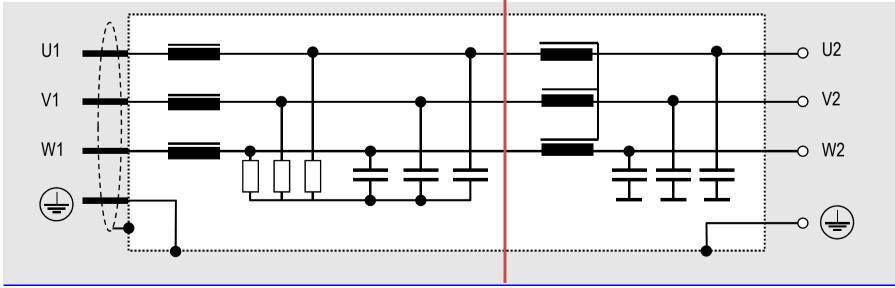- Common-mode current reduction
- Field strength reduction
- Conducted emission reduction




Measurements of the converter output

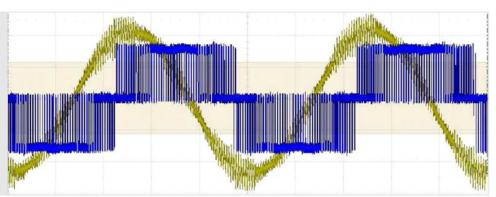- Phase-to-phase voltage is not sinusoidal
 - → Creation of interferences and bearing currents



Measurements of the filter output (300 m motor line)

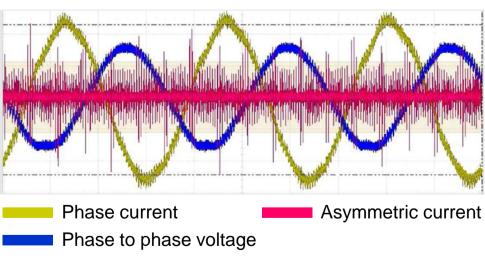
- Phase-to-phase voltage is sinusoidal
- Asymmetric (common-mode) current significantly reduced



No shielded motor cable required, bearing currents minimized!



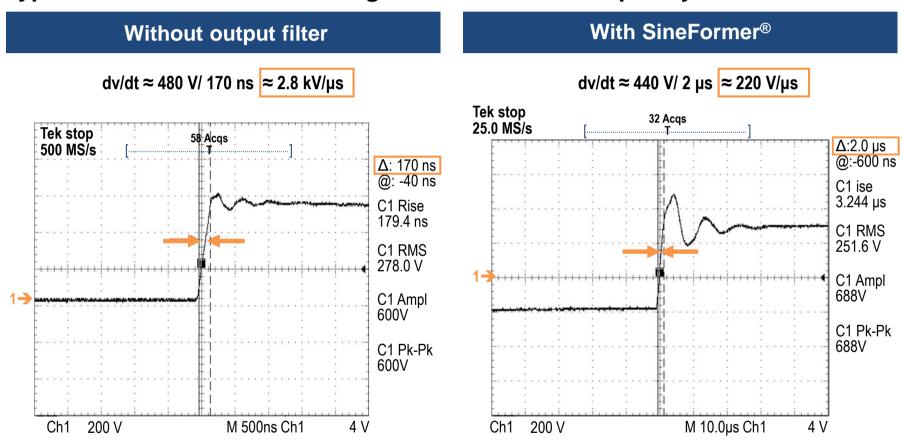
Typical value for 4 kHz switching and 50 Hz motor frequency



dv/dt peaks reduced significantly to uncritical values



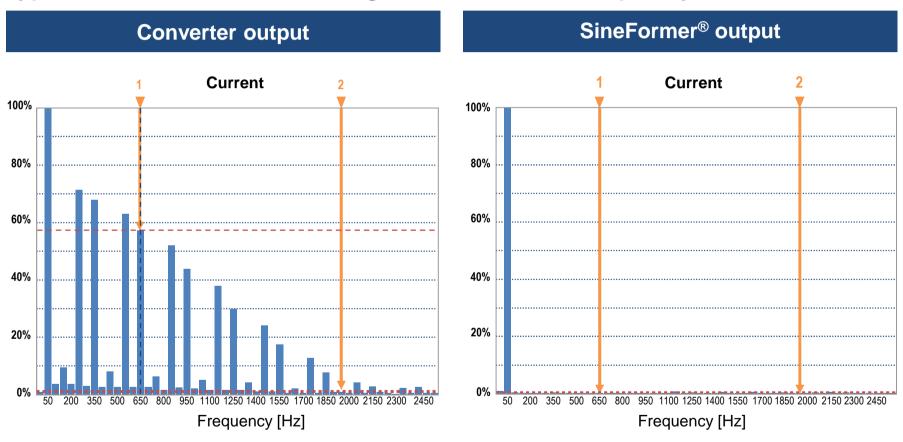Typical value for 4 kHz switching and 50 Hz motor frequency




Elimination of harmonics on the output side!

Converter and unshielded cable (without SineFormer®)


Limits exceeded

Limits kept

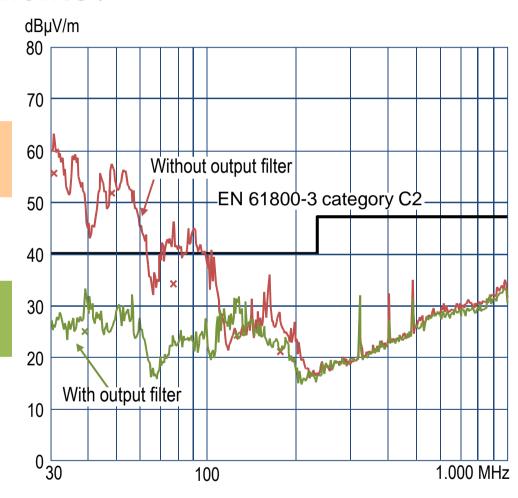Converter and unshielded cable (with SineFormer®)



Field strength: Goodbye shielded cables!

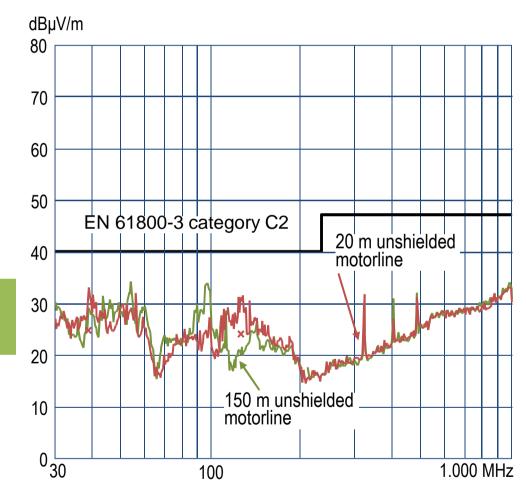


Coherent results at different motor cable lengths

Field strength performance is not dependent on cable length!

Radiation measurement vertical antenna (worst case)

- Converter 2.2 kW/ 400 V
- Filter 11 A
- 300 m motor cable
- 8 kHz clock frequency

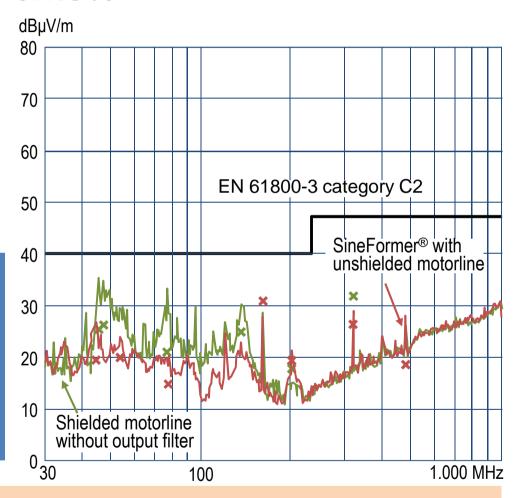With an increase of the cable cross section, this effect will be even higher because the shielding will be more coarsely meshed.





SineFormer® + unshielded motor cable have better performance than shielded motor cables!

Bearing current measurements with sine-wave filters

Measurement bearing current with sine-wave filter

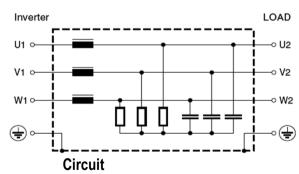- Drive 2.2 kW/ 400 V
- 25 m motor line
- 4 kHz clock frequency
- 5 Hz motor frequency



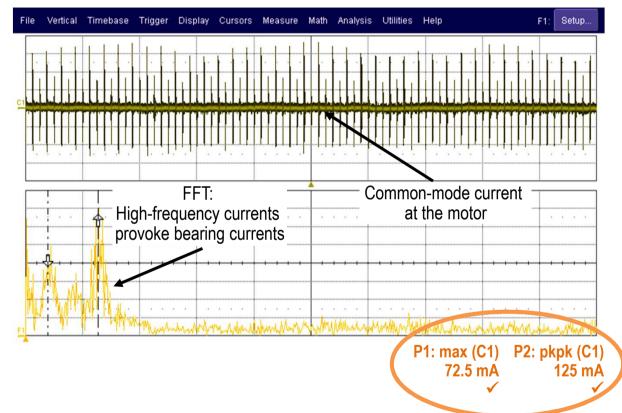



Sine-wave filters only partially reduce bearing currents in the motor!

Bearing current measurements with SineFormer®

Measurement bearing current with SineFormer®

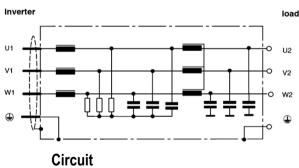- Drive 2.2 kW/ 400 V
- 25 m motor line
- 4 kHz clock frequency
- 5 Hz motor frequency



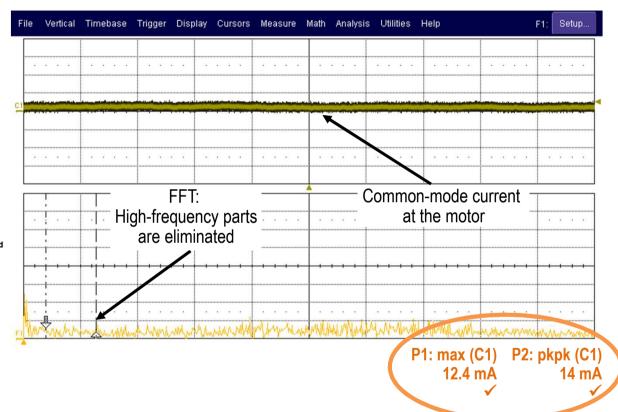

Only SineFormer® filters reduce bearing currents significantly!



www.SineFormer.com